



Grade Sheet for Lab #1

Fall 2016.

Group Number: 07

Group Member Name: JAHN LEE

Group Member Name: ANDREW LOWMYER

Student Number: 260633759

Student Number: 260558337

Marks

2
2
2
2
2
2
2

1. Schematic diagram for the 6-bit comparator
2. VHDL file for the 6-bit comparator
3. Initial partial simulation results for the 6-bit comparator
4. Complete simulation results for the 6-bit comparator
5. VHDL description for the 16:4 encoder circuit
6. Simulation Testbench VHDL for the 16:4 encoder circuit
7. Simulation results for the 16:4 encoder circuit

TA Signatures

Each part should be demonstrated to one of the TAs who will then give a grade and sign the grade sheet. Grades for each part will be either 0, 1, or 2. A mark of 2 will be given if everything is done correctly. A grade of 1 will be given if there are significant problems, but an attempt was made. A grade of 0 will be given for parts that were not done at all, or for which there is no TA signature.

